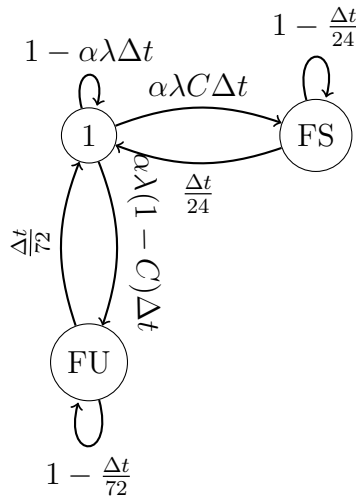


# Fault Tolerant Computing and VLSI Testing

## Assignment 3

1. The Markov Model for the system with self-diagnostics is:



- 1 is where the system is working successfully.
- FS is where a fault has been detected and the system has been safely deactivated.
- FU is where a fault has not been detected.

The Mean Time To Failure (MTTF) will be the amount of time we expect to stay in the working state. This is the value of  $t$  such that  $t\alpha\lambda = 1$ . This is equal to  $t = \frac{1}{\lambda\alpha}$


We detect the failure with probability 0.95, and don't with probability 0.05. This gives us a mean time between failures of:

$$0.95 * 24 + 0.05 * 72 = 26.4$$

Thus, the steady-state availability is:

$$A = \frac{1}{\alpha\lambda(\frac{1}{\alpha\lambda} + 26.4)} = \frac{1}{1 + 26.4\alpha\lambda}$$

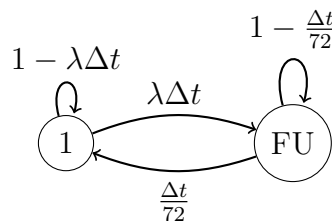The Markov Model for the system without self-diagnostics is:



- 1 is where the system is working successfully.
- FU is where a fault has occurred.

The MTTF is  $\frac{1}{\lambda}$  and the steady-state availability is:


$$A = \frac{1}{\lambda(\frac{1}{\lambda} + 72)} = \frac{1}{1 + 72\lambda}$$

We can find the value of  $\alpha$  for which self-diagnostics begins to degrade the steady-state availability by equating these two equations:


$$\frac{1}{1 + 26.4\alpha\lambda} = \frac{1}{1 + 72\lambda} \implies 1 + 26.4\alpha\lambda = 1 + 72\lambda \implies 26.4\alpha\lambda = 72\lambda$$

$$\alpha = \frac{72}{26.4} = 2.727$$

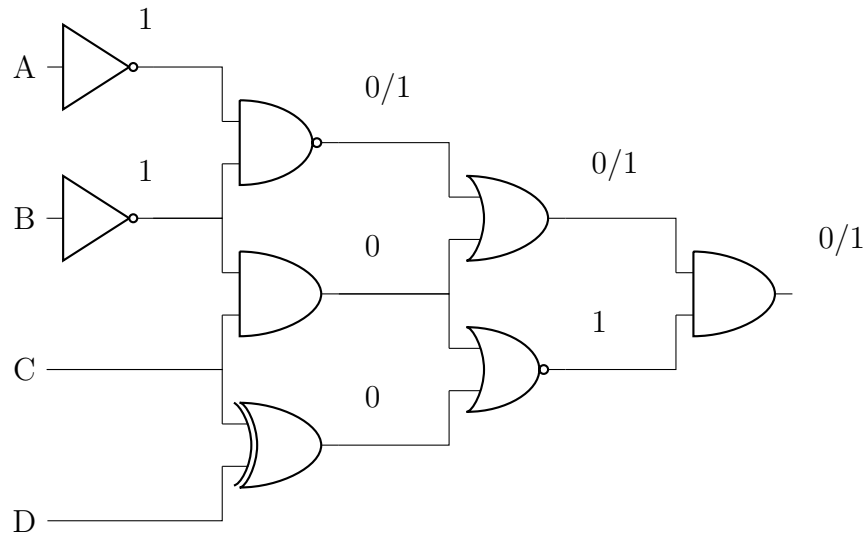
2. (i)  $ABCD = 0000$  can detect line 4 stuck-at 0:



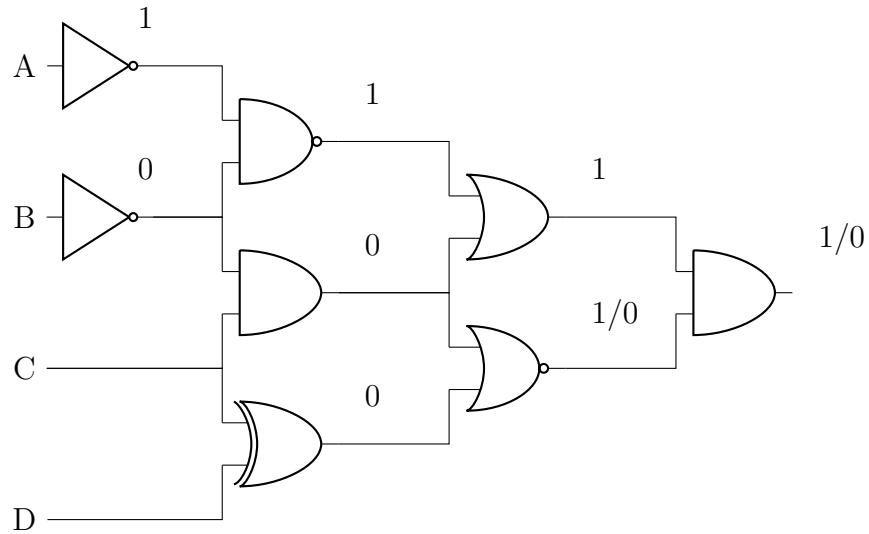- (ii)  $ABCD = 0100$  can detect line 13 stuck-at 1:



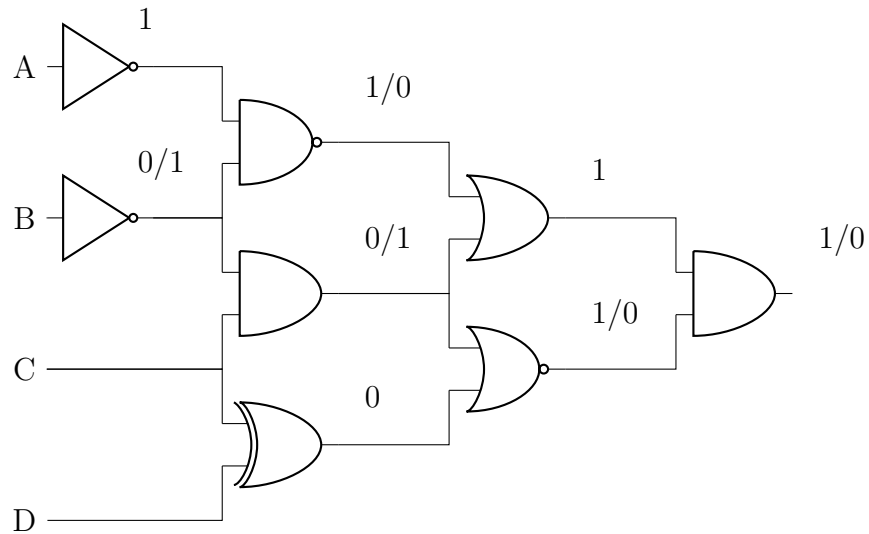(iii)  $ABCD = 0111$  can detect input B stuck-at 0:



$$3. FC = 80\% \Rightarrow DL = 1 - 0.9^{1-0.8} = 0.020852 = 20852PPM$$

$$FC = 90\% \Rightarrow DL = 1 - 0.9^{1-0.9} = 0.010481 = 10481PPM$$

$$FC = 99\% \Rightarrow DL = 1 - 0.9^{1-0.99} = 0.001053 = 1053PPM$$

$$DL = 20PPM = 2 * 10^{-5} = 1 - 0.6^{1-FC}$$

$$0.6^{1-FC} = 1 - 2 * 10^{-5} = 0.99998$$

$$1 - FC = \log_{0.6} 0.99998 = 3.915 * 10^{-5}$$


$$FC = 1 - 3.915 * 10^{-5} = 0.99996 = 99.996\%$$

4.

AB	00	01	10	11
Z	1	1	1	0
$P_0$ stuck open	1	LastZ	1	0
$P_0$ stuck short	1	1	1	$I_{DDQ}$
$P_1$ stuck open	1	1	LastZ	0
$P_1$ stuck short	1	1	1	$I_{DDQ}$
$N_0$ stuck open	1	1	1	LastZ
$N_0$ stuck short	1	$I_{DDQ}$	1	0
$N_1$ stuck open	1	1	1	LastZ
$N_1$ stuck short	1	1	$I_{DDQ}$	0

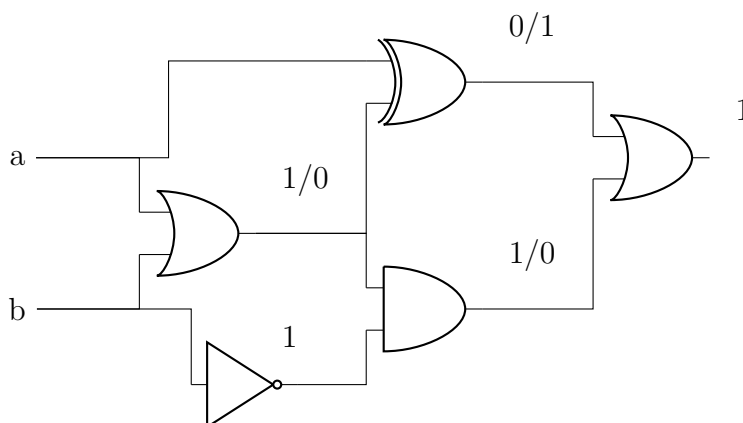5. (1) Note that  $a = 1$  in order to exercise d sa0, as that is the only input that can set the wire d to 1. Also note that  $b = 0$ , as otherwise the fault d sa0 will have no effect after the OR-gate.

Therefore the only input that could test this fault is  $ab = 10$ . Here is what this input produces:



So even with this input, the fault d sa0 cannot be detected. The fault is therefore redundant.


We can remove the redundancy by considering the operation of the circuit:

$$a \oplus (a + b) = a\overline{(a + b)} + \overline{a}(a + b) = a\overline{a}\overline{b} + \overline{a}a + \overline{a}b = \overline{a}b$$


$$(a + b)\overline{b} = a\overline{b} + b\overline{b} = a\overline{b}$$

$$(a \oplus (a + b)) + (a + b)\overline{b} = \overline{a}b + a\overline{b}$$

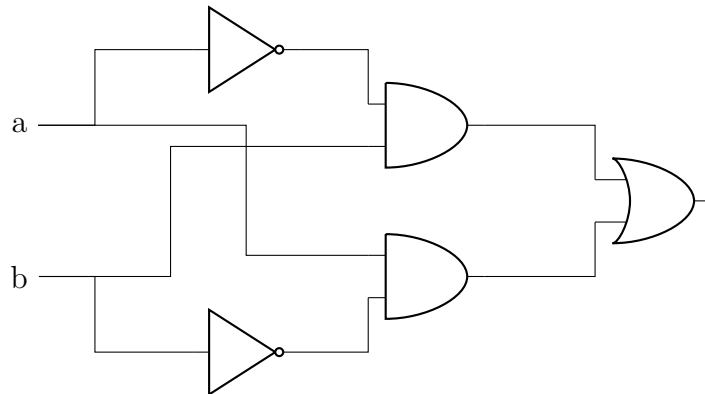
Our redundancy-free circuit is therefore the following:



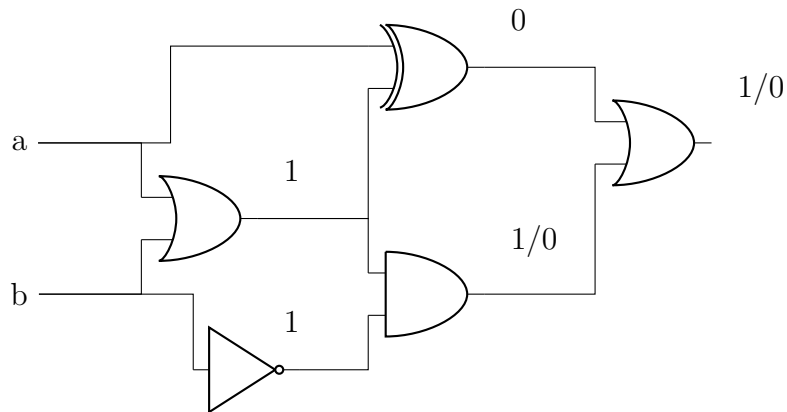(2)  $ab = 10$  can detect the fault in  $sa0$ :



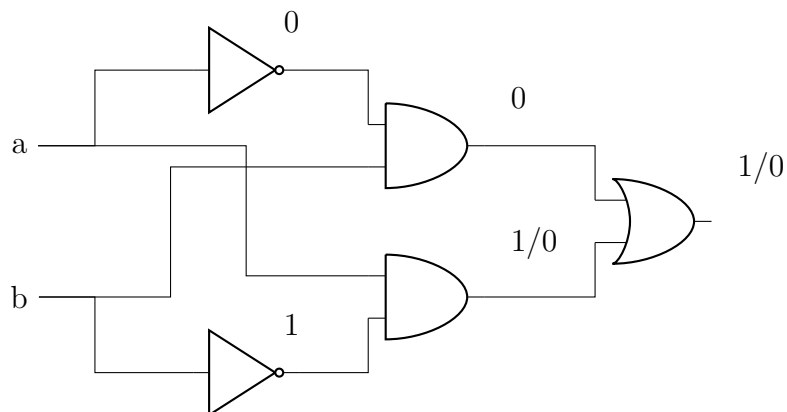
The wire  $m$  fed in the original circuit fed into the reduced AND operation  $a\bar{b}$ . The gate for this operation is still in the redundancy-free circuit, so we can still test for this fault by testing the  $a$  input for the AND gate.  $ab = 10$  can detect the fault in this wire too:



As stated above, the operation is equivalent to:

$$\bar{a}b + a\bar{b} = a \oplus b$$

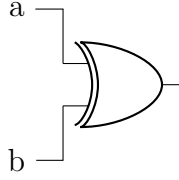Therefore, the boolean operation this circuit is equivalent to is exclusive-OR. The minimum implementation is:



6. Note that a  $*$  symbol is used where appropriate to represent the AND operation for clarity, in order to help distinguish between, for example,  $\overline{a} * \overline{c}$  and  $\overline{a} * \overline{c}$

$$\begin{aligned} \text{(i)} \quad \overline{a} \frac{dz}{da} &= \overline{a}(z(a=1) \oplus z(a=0)) = \overline{a}((\overline{c} + cb) \oplus cb) \\ &= \overline{a}(\overline{c} + \overline{cbcb} + (\overline{c} + cb)\overline{cb}) = \overline{a}(\overline{c}\overline{cbcb} + \overline{c}\overline{cb} + cb\overline{cb}) \\ &= \overline{a} * \overline{c}\overline{cb} = \overline{a} * \overline{c}(\overline{c} + \overline{b}) = \overline{a} * \overline{c} + \overline{a} * \overline{c}\overline{b} = \overline{a} * \overline{c}(1 + \overline{b}) = \overline{a} * \overline{c} = 1 \end{aligned}$$

The patterns  $abc = 000, 010$  can detect the fault line a s-a-1.

$$\begin{aligned} \text{(ii)} \quad h \frac{dz}{dh} &= h(z(h=1) \oplus z(h=0)) = h(1 \oplus a\overline{c}) = h\overline{a}\overline{c} = h(\overline{a} + c) \\ &= h\overline{a} + hc \end{aligned}$$

Note that  $h = cb$ .

$$h \frac{dz}{dh} = \overline{a}bc + bc = bc(a + 1) = bc = 1$$

The patterns  $abc = 011, 111$  can detect the fault line h s-a-0.

$$\begin{aligned} \text{(iii)} \quad \overline{h} \frac{dz}{dh} &= \overline{h}\overline{a} + \overline{h}c = \overline{cb}\overline{a} + \overline{cb}c = (\overline{c} + \overline{b})\overline{a} + (\overline{c} + \overline{b})c \\ &= \overline{a}\overline{b} + \overline{a}\overline{c} + \overline{b}c + \overline{c}c = \overline{a}\overline{b} + \overline{a} * \overline{c} + \overline{b}c = 1 \end{aligned}$$

The patterns  $abc = 000, 001, 010, 101$  can detect the fault line h s-a-1.

$$\begin{aligned} \text{(iv)} \quad e \frac{dz}{de} &= e(z(e=1) \oplus z(e=0)) = e((a\overline{c} + b) \oplus a\overline{c}) \\ &= e(\overline{a\overline{c} + b}a\overline{c} + (a\overline{c} + b)\overline{a\overline{c}}) = e(\overline{b} * \overline{a\overline{c}a\overline{c}} + a\overline{c}\overline{a\overline{c}} + b\overline{a\overline{c}}) = e\overline{b}\overline{a\overline{c}} \\ &= be(\overline{a} + c) = \overline{a}be + bec \end{aligned}$$

Note that  $e = c$ .

$$e \frac{dz}{de} = \overline{a}bc + bc = bc(\overline{a} + 1) = bc = 1$$

The patterns  $abc = 011, 111$  can detect the fault line e s-a-0.

$$\text{(v)} \quad \overline{e} \frac{dz}{de} = \overline{a}\overline{b}\overline{e} + \overline{b}\overline{e}c = \overline{a}\overline{b}\overline{c} + bc\overline{c} = \overline{a}\overline{b}\overline{c}$$

The pattern  $abc = 010$  can detect the fault line e s-a-1.

$$\text{(vi)} \quad c \frac{dz}{dc} = c(z(c=1) \oplus z(c=0)) = c(b \oplus a) = c(\overline{a}b + a\overline{b}) = \overline{a}bc + a\overline{b}c = 1$$

The patterns  $abc = 011, 101$  can detect the fault line c s-a-0.

7. (a)  $\bar{a} \frac{di}{da} = \bar{a}(i(a=1) \oplus i(a=0)) = \bar{a}(b \oplus 0) = \bar{a}b = 1$

The pattern  $ab = 01$  can detect the fault  $a/1$ .

(b)  $\bar{d} \frac{di}{da} = \bar{d}(i(d=1) \oplus i(d=0)) = \bar{d}(ab \oplus 0) = \bar{d}ab$

Note that  $d = a$ .

$$\bar{d} \frac{di}{da} = \bar{a}ab = 0 = 1$$

We have reached a contradiction, therefore the fault  $d/1$  cannot be detected.

(c)  $\bar{g} \frac{di}{dg} = \bar{g}(i(g=1) \oplus i(g=0)) = \bar{g}(ab \oplus 0) = \bar{g}ab$

Note that  $g = ab$ .

$$\bar{g} \frac{di}{dg} = \bar{a}bab = 0 = 1$$

We have reached a contradiction, therefore the fault  $g/1$  cannot be detected.

8. Below are the signatures calculated for the sequence  $M = 10011011$  (fault-free) and the faulty sequence  $M' = 11111111$

$M$	$R_1$	$R_2$	$R_3$	$R_4$	$M'$	$R_1$	$R_2$	$R_3$	$R_4$
1	0	0	0	0	1	0	0	0	0
1	1	0	0	0	1	1	0	0	0
0	1	1	0	0	1	1	1	0	0
1	0	1	1	0	1	1	1	1	0
1	1	0	1	1	1	1	1	1	1
0	0	0	0	1	1	0	0	1	1
0	1	1	0	0	1	0	1	0	1
1	0	1	1	0	1	0	1	1	0
$R$	1	0	1	1	$R$	1	0	1	1

The signature for the faulty sequence  $M'$  matches the signature for the fault-free sequence  $M$ , so this fault is not detected.