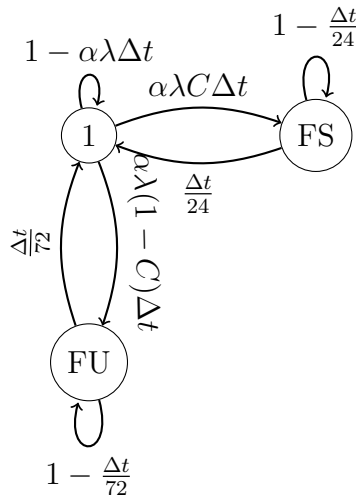


Fault Tolerant Computing and VLSI Testing

Assignment 3

1. The Markov Model for the system with self-diagnostics is:



- 1 is where the system is working successfully.
- FS is where a fault has been detected and the system has been safely deactivated.
- FU is where a fault has not been detected.

The Mean Time To Failure (MTTF) will be the amount of time we expect to stay in the working state. This is the value of t such that $t\alpha\lambda = 1$. This is equal to $t = \frac{1}{\lambda\alpha}$


We detect the failure with probability 0.95, and don't with probability 0.05. This gives us a Mean Time To Repair (MTTR) of:

$$0.95 * 24 + 0.05 * 72 = 26.4$$

Thus, the steady-state availability is:

$$A = \frac{1}{\alpha\lambda(\frac{1}{\alpha\lambda} + 26.4)} = \frac{1}{1 + 26.4\alpha\lambda}$$

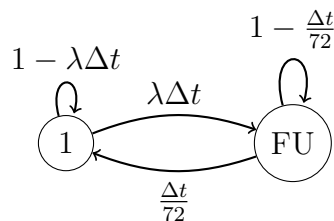The Markov Model for the system without self-diagnostics is:



- 1 is where the system is working successfully.
- FU is where a fault has occurred.

The MTTF is $\frac{1}{\lambda}$ and the steady-state availability is:


$$A = \frac{1}{\lambda(\frac{1}{\lambda} + 72)} = \frac{1}{1 + 72\lambda}$$

We can find the value of α for which self-diagnostics begins to degrade the steady-state availability by equating these two equations:


$$\frac{1}{1 + 26.4\alpha\lambda} = \frac{1}{1 + 72\lambda} \implies 1 + 26.4\alpha\lambda = 1 + 72\lambda \implies 26.4\alpha\lambda = 72\lambda$$

$$\alpha = \frac{72}{26.4} = 2.727$$

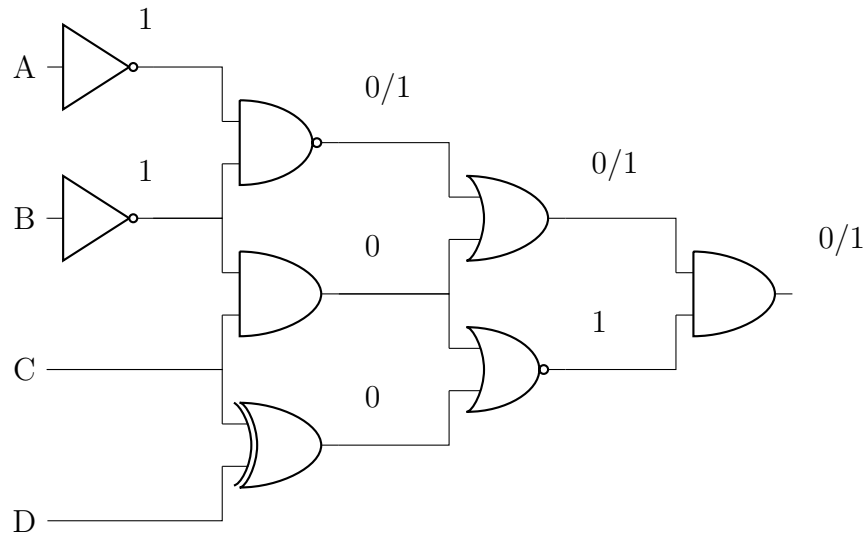
2. (i) $ABCD = 0000$ can detect line 4 stuck-at 0:



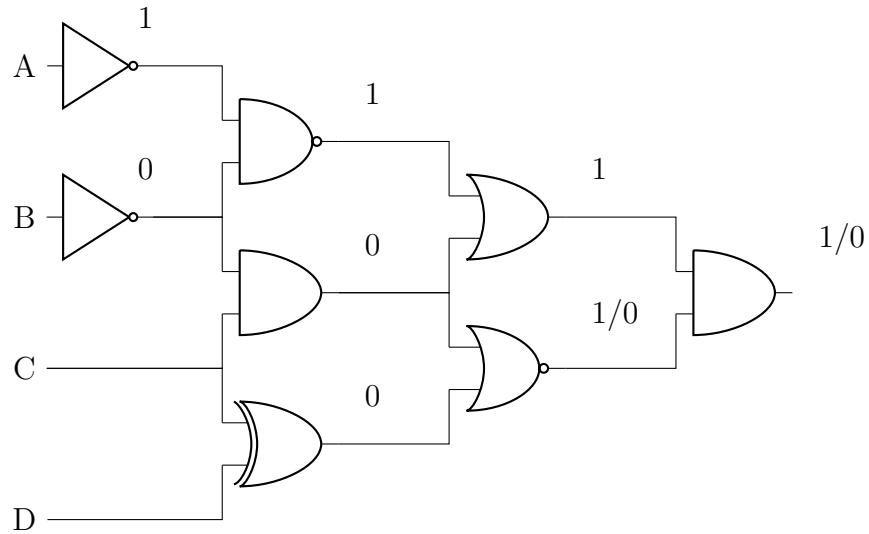- (ii) $ABCD = 0100$ can detect line 13 stuck-at 1:



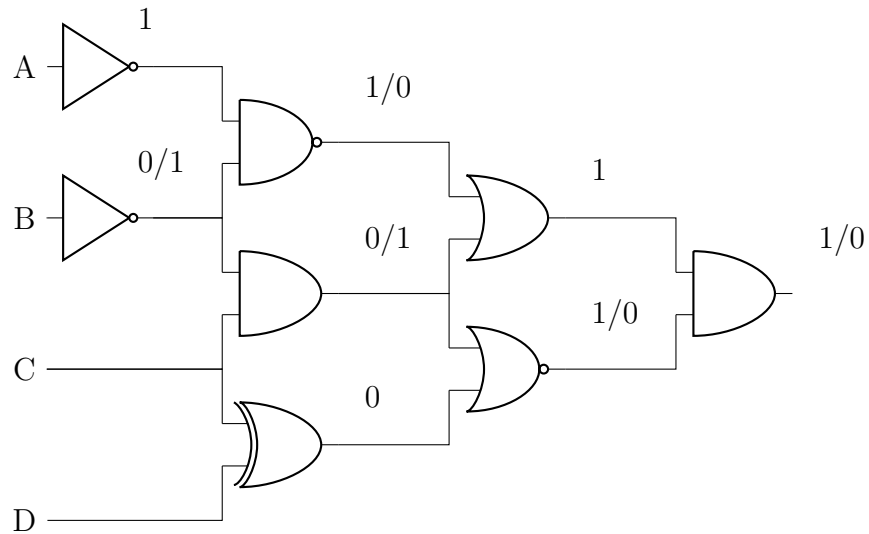(iii) $ABCD = 0111$ can detect input B stuck-at 0:



$$3. \quad FC = 80\% \Rightarrow DL = 1 - 0.9^{1-0.8} = 0.020852 = 20852PPM$$

$$FC = 90\% \Rightarrow DL = 1 - 0.9^{1-0.9} = 0.010481 = 10481PPM$$


$$FC = 99\% \Rightarrow DL = 1 - 0.9^{1-0.99} = 0.001053 = 1053PPM$$

$$DL = 20PPM = 2 * 10^{-5} = 1 - 0.6^{1-FC}$$


$$0.6^{1-FC} = 1 - 2 * 10^{-5} = 0.99998$$

$$1 - FC = \log_{0.6} 0.99998 = 3.915 * 10^{-5}$$

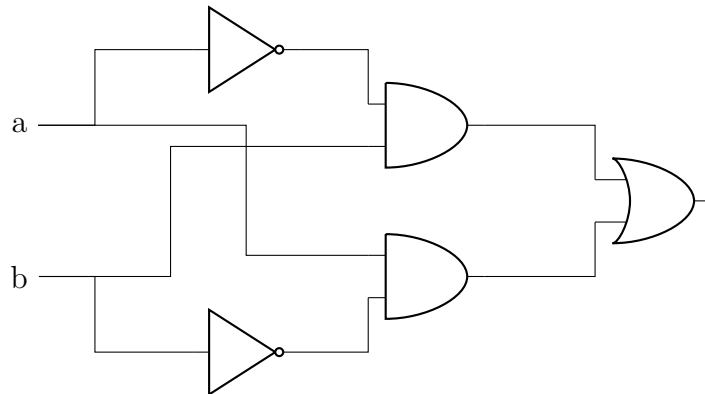
$$FC = 1 - 3.915 * 10^{-5} = 0.99996 = 99.996\%$$



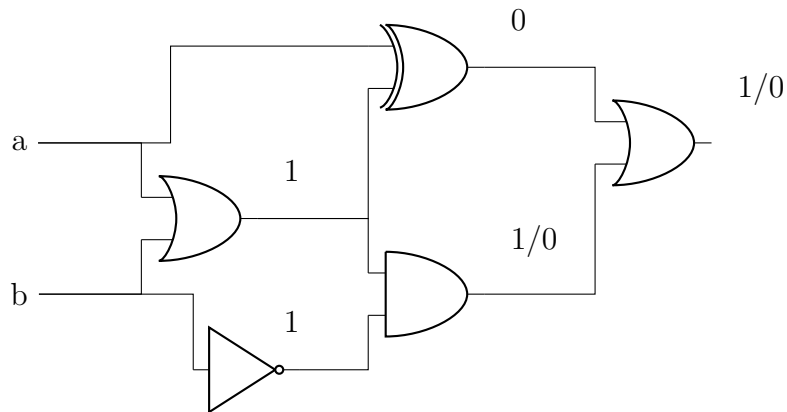(2) $ab = 10$ can detect the fault m sa0:



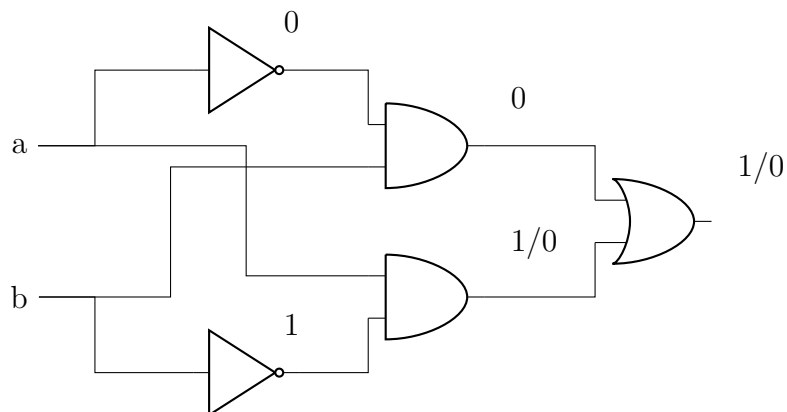
The wire m fed in the original circuit fed into the reduced AND operation $a\bar{b}$. The gate for this operation is still in the redundancy-free circuit, so we can still test for this fault by testing the a input for the AND gate. $ab = 10$ can detect the fault in this wire too:



As stated above, the operation is equivalent to:

$$\bar{a}b + a\bar{b} = a \oplus b$$

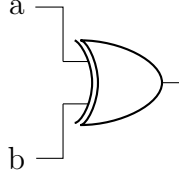Therefore, the boolean operation this circuit is equivalent to is exclusive-OR. The minimum implementation is:



6. Note that a $*$ symbol is used where appropriate to represent the AND operation for clarity, in order to help distinguish between, for example, $\overline{a} * \overline{c}$ and $\overline{a * c}$

$$\begin{aligned} \text{(i)} \quad \overline{a} \frac{dz}{da} &= \overline{a}(z(a=1) \oplus z(a=0)) = \overline{a}((\overline{c} + cb) \oplus cb) \\ &= \overline{a}(\overline{c} + \overline{cbcb} + (\overline{c} + cb)\overline{cb}) = \overline{a}(\overline{c}\overline{cbcb} + \overline{c}\overline{cb} + cb\overline{cb}) \\ &= \overline{a} * \overline{c}\overline{cb} = \overline{a} * \overline{c}(\overline{c} + \overline{b}) = \overline{a} * \overline{c} + \overline{a} * \overline{c}\overline{b} = \overline{a} * \overline{c}(1 + \overline{b}) = \overline{a} * \overline{c} = 1 \end{aligned}$$

The patterns $abc = 000, 010$ can detect the fault line a s-a-1.

$$\begin{aligned} \text{(ii)} \quad h \frac{dz}{dh} &= h(z(h=1) \oplus z(h=0)) = h(1 \oplus a\overline{c}) = h\overline{a}\overline{c} = h(\overline{a} + c) \\ &= h\overline{a} + hc \end{aligned}$$

Note that $h = cb$.

$$h \frac{dz}{dh} = \overline{a}bc + bc = bc(a+1) = bc = 1$$

The patterns $abc = 011, 111$ can detect the fault line h s-a-0.

$$\begin{aligned} \text{(iii)} \quad \overline{h} \frac{dz}{dh} &= \overline{h}\overline{a} + \overline{h}c = \overline{cb}\overline{a} + \overline{cb}c = (\overline{c} + \overline{b})\overline{a} + (\overline{c} + \overline{b})c \\ &= \overline{a}\overline{b} + \overline{a}\overline{c} + \overline{b}c + \overline{c}c = \overline{a}\overline{b} + \overline{a} * \overline{c} + \overline{b}c = 1 \end{aligned}$$

The patterns $abc = 000, 001, 010, 101$ can detect the fault line h s-a-1.

$$\begin{aligned} \text{(iv)} \quad e \frac{dz}{de} &= e(z(e=1) \oplus z(e=0)) = e((a\overline{c} + b) \oplus a\overline{c}) \\ &= e(\overline{a\overline{c} + b}a\overline{c} + (a\overline{c} + b)\overline{a\overline{c}}) = e(\overline{b} * \overline{a\overline{c}a\overline{c}} + a\overline{c}\overline{a\overline{c}} + b\overline{a\overline{c}}) = e\overline{b}\overline{a\overline{c}} \\ &= be(\overline{a} + c) = \overline{a}be + bec \end{aligned}$$

Note that $e = c$.

$$e \frac{dz}{de} = \overline{a}bc + bc = bc(\overline{a} + 1) = bc = 1$$

The patterns $abc = 011, 111$ can detect the fault line e s-a-0.

$$\text{(v)} \quad \overline{e} \frac{dz}{de} = \overline{a}\overline{b}\overline{e} + \overline{b}\overline{e}c = \overline{a}\overline{b}\overline{c} + bc\overline{c} = \overline{a}\overline{b}\overline{c}$$

The pattern $abc = 010$ can detect the fault line e s-a-1.

$$\text{(vi)} \quad c \frac{dz}{dc} = c(z(c=1) \oplus z(c=0)) = c(b \oplus a) = c(\overline{a}b + a\overline{b}) = \overline{a}bc + a\overline{b}c = 1$$

The patterns $abc = 011, 101$ can detect the fault line c s-a-0.

7. (a) $\bar{a} \frac{di}{da} = \bar{a}(i(a=1) \oplus i(a=0)) = \bar{a}(b \oplus 0) = \bar{a}b = 1$

The pattern $ab = 01$ can detect the fault a/1.

(b) $\bar{d} \frac{di}{da} = \bar{d}(i(d=1) \oplus i(d=0)) = \bar{d}(ab \oplus 0) = \bar{d}ab$

Note that $d = a$.

$$\bar{d} \frac{di}{da} = \bar{a}ab = 0 = 1$$

We have reached a contradiction, therefore the fault d/1 cannot be detected.

(c) $\bar{g} \frac{di}{dg} = \bar{g}(i(g=1) \oplus i(g=0)) = \bar{g}(ab \oplus 0) = \bar{g}ab$

Note that $g = ab$.

$$\bar{g} \frac{di}{dg} = \bar{a}bab = 0 = 1$$

We have reached a contradiction, therefore the fault g/1 cannot be detected.

8. Below are the signatures calculated for the sequence $M = 10011011$ (fault-free) and the faulty sequence $M' = 11111111$

M	R_1	R_2	R_3	R_4	M'	R_1	R_2	R_3	R_4
1	0	0	0	0	1	0	0	0	0
1	1	0	0	0	1	1	0	0	0
0	1	1	0	0	1	1	1	0	0
1	0	1	1	0	1	1	1	1	0
1	1	0	1	1	1	1	1	1	1
0	0	0	0	1	1	0	0	1	1
0	1	1	0	0	1	0	1	0	1
1	0	1	1	0	1	0	1	1	0
R	1	0	1	1	R	1	0	1	1

The signature for the faulty sequence M' matches the signature for the fault-free sequence M , so this fault is not detected.