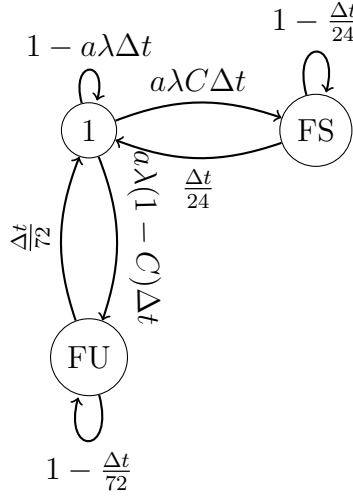


# Fault Tolerant Computing and VLSI Testing

## Assignment 3

1. The Markov Model for the system with self-diagnostics is:



- 1 is where the system is working successfully.
- FS is where a fault has been detected and the system has been safely deactivated.
- FU is where a fault has not been detected.

$$P(t) = \begin{bmatrix} P_1(t) \\ P_{FS}(t) \\ P_{FU}(t) \end{bmatrix}, P_1(t) + P_{FS}(t) + P_{FU}(t) = 1, P(0) = \begin{bmatrix} 1 \\ 0 \\ 0 \end{bmatrix}$$

$$A = \begin{bmatrix} 1 - a\lambda\Delta t & \frac{\Delta t}{24} & \frac{\Delta t}{72} \\ a\lambda C\Delta t & 1 - \frac{\Delta t}{24} & 0 \\ a\lambda(1 - C)\Delta t & 0 & 1 - \frac{\Delta t}{72} \end{bmatrix}$$

$$P(t + \Delta t) = AP(t) = \begin{bmatrix} P_1(t)(1 - a\lambda\Delta t) + P_{FS}(t)\frac{\Delta t}{24} + P_{FU}(t)\frac{\Delta t}{72} \\ P_1(t)a\lambda C\Delta t + P_{FS}(t)(1 - \frac{\Delta t}{24}) \\ P_1(t)a\lambda(1 - C)\Delta t + P_{FU}(t)(1 - \frac{\Delta t}{72}) \end{bmatrix}$$

$$P_1(t + \Delta t) = P_1(t)(1 - a\lambda\Delta t) + P_{FS}(t)\frac{\Delta t}{24} + P_{FU}(t)\frac{\Delta t}{72}$$

$$P_{FS}(t + \Delta t) = P_1(t)a\lambda C\Delta t + P_{FS}(t)(1 - \frac{\Delta t}{24})$$

$$P_{FU}(t + \Delta t) = P_1(t)a\lambda(1 - C)\Delta t + P_{FU}(t)(1 - \frac{\Delta t}{72})$$

$$\frac{P_1(t + \Delta t) - P_1(t)}{\Delta t} = -P_1(t)a\lambda + \frac{P_{FS}(t)}{24} + \frac{P_{FU}(t)}{72}$$

$$\frac{P_{FS}(t+\Delta t) - P_{FS}(t)}{\Delta t} = P_1(t)a\lambda C - \frac{P_{FS}(t)}{24}$$

$$\frac{P_{FU}(t+\Delta t) - P_{FU}(t)}{\Delta t} = P_1(t)a\lambda(1 - C) - \frac{P_{FU}(t)}{72}$$


As  $\Delta t \rightarrow 0$ :

$$\frac{dP_1(t)}{dt} = -P_1(t)a\lambda + \frac{P_{FS}(t)}{24} + \frac{P_{FU}(t)}{72}$$

$$\frac{dP_{FS}(t)}{dt} = P_1(t)a\lambda C - \frac{P_{FS}(t)}{24}$$

$$\frac{dP_{FU}(t)}{dt} = P_1(t)a\lambda(1 - C) - \frac{P_{FU}(t)}{72}$$

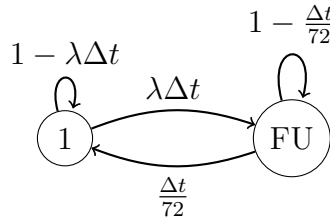The Markov Model for the system without self-diagnostics is:



- 1 is where the system is working successfully.
- FU is where a fault has occurred.

$$P(t) = \begin{bmatrix} P_1(t) \\ P_{FU}(t) \end{bmatrix}, P_1(t) + P_{FU}(t) = 1, P(0) = \begin{bmatrix} 1 \\ 0 \end{bmatrix}, A = \begin{bmatrix} 1 - \lambda\Delta t & \frac{\Delta t}{72} \\ \lambda\Delta t & 1 - \frac{\Delta t}{72} \end{bmatrix}$$

$$P(t + \Delta t) = AP(t) = \begin{bmatrix} P_1(t)(1 - \lambda\Delta t) + P_{FU}(t)\frac{\Delta t}{72} \\ P_1(t)\lambda\Delta t + P_{FU}(t)(1 - \frac{\Delta t}{72}) \end{bmatrix}$$

$$\frac{P_1(t+\Delta t) - P_1(t)}{\Delta t} = -P_1(t)\lambda + \frac{P_{FU}(t)}{72}, \frac{P_{FU}(t+\Delta t) - P_{FU}(t)}{\Delta t} = P_1(t)\lambda - \frac{P_{FU}(t)}{72}$$

As  $\Delta t \rightarrow 0$ :

$$\frac{dP_1(t)}{dt} = -P_1(t)\lambda + \frac{P_{FU}(t)}{72}, \frac{dP_{FU}(t)}{dt} = P_1(t)\lambda - \frac{P_{FU}(t)}{72}$$

$$sP_1(s) + sP_{FU}(s) = 1 \implies P_{FU}(s) = \frac{1 - sP_1(s)}{s}$$

$$sP_1(s) - P_1(0) = sP_1(s) - 1 = -P_1(s)\lambda + \frac{P_{FU}(s)}{72} = -P_1(s)\lambda + \frac{1 - sP_1(s)}{72s}$$

$$s^2P_1(s) - s = -sP_1(s)\lambda + \frac{1 - sP_1(s)}{72}$$

$$s^2P_1(s) + sP_1(s)\lambda + \frac{sP_1(s)}{72} = sP_1(s)(s + \lambda + \frac{1}{72}) = s + \frac{1}{72}$$

$$P_1(s) = \frac{s + \frac{1}{72}}{(s)(s + \lambda + \frac{1}{72})}$$

We can solve this equation via partial fractions:

$$P_1(s) = \frac{s + \frac{1}{72}}{(s)(s + \lambda + \frac{1}{72})} = \frac{A}{s} + \frac{B}{s + \lambda + \frac{1}{72}} \implies A(s + \lambda + \frac{1}{72}) + Bs = s + \frac{1}{72}$$

$$s = 0 \implies A(\lambda + \frac{1}{72}) = \frac{1}{72} \implies A = \frac{1}{72(\lambda + \frac{1}{72})}$$


$$s = -(\lambda + \frac{1}{72}) \implies -B(\frac{1}{72} + \lambda) = -\lambda \implies B = \frac{\lambda}{\frac{1}{72} + \lambda}$$

$$P_1(s) = \frac{1}{72(\lambda + \frac{1}{72})s} + \frac{\lambda}{(\frac{1}{72} + \lambda)(s + \lambda + \frac{1}{72})}$$


$$R(t) = P_1(t) = \frac{1}{72(\lambda + \frac{1}{72})} + \frac{\lambda}{\frac{1}{72} + \lambda} e^{-(\lambda + \frac{1}{72})t} = \frac{1}{72\lambda + 1} + \frac{\lambda}{\frac{1}{72} + \lambda} e^{-(\lambda + \frac{1}{72})t}$$

2. Test patterns are written as  $ABCD$


(i) 0000

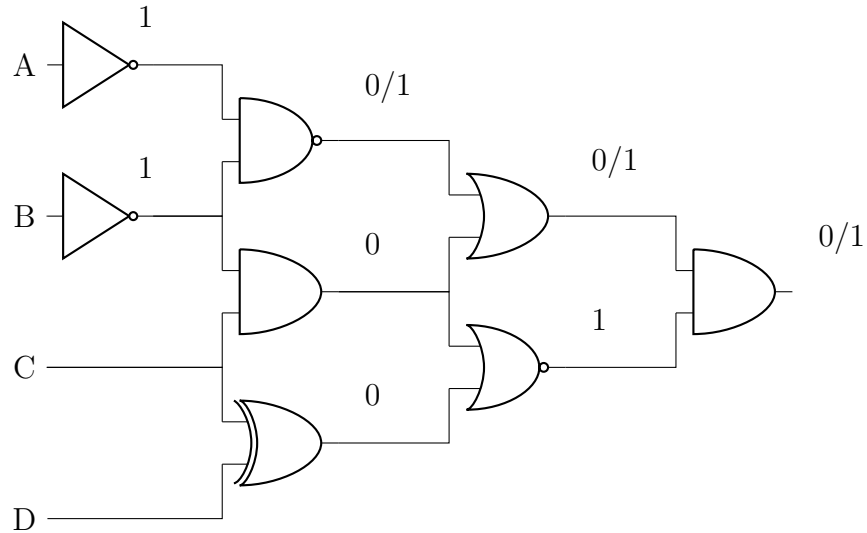

(ii) 0100

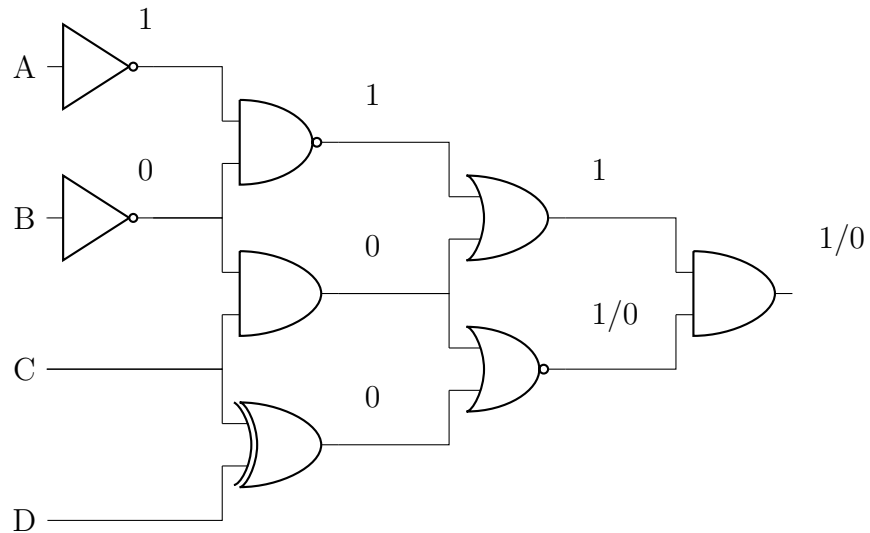

(iii) 0111

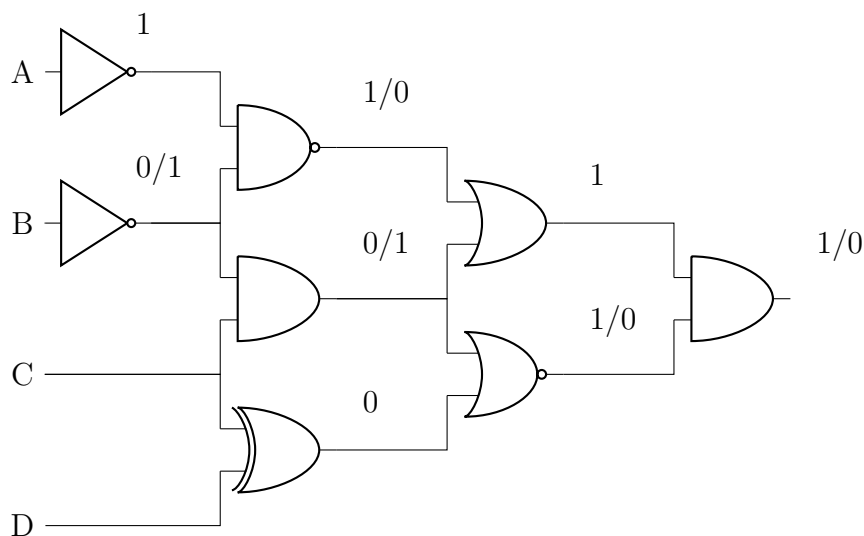

3.  $FC = 80\% \Rightarrow DL = 1 - 0.9^{1-0.8} = 0.020852 = 20852PPM$

$FC = 90\% \Rightarrow DL = 1 - 0.9^{1-0.9} = 0.010481 = 10481PPM$

$FC = 99\% \Rightarrow DL = 1 - 0.9^{1-0.99} = 0.001053 = 1053PPM$

$DL = 20PPM = 2 * 10^{-5} = 1 - 0.7^{1-FC}$

$0.6^{1-FC} = 1 - 2 * 10^{-5} = 0.99998$

$1 - FC = \log_{0.6} 0.99998 = 3.915 * 10^{-5}$


$FC = 1 - 3.915 * 10^{-5} = 0.99996 = 99.996\%$

4.

AB	00	01	10	11
Z	1	1	1	0
$P_0$ stuck open	1	LastZ	1	0
$P_0$ stuck short	1	1	1	$I_{DDQ}$
$P_1$ stuck open	1	1	LastZ	0
$P_1$ stuck short	1	1	1	$I_{DDQ}$
$N_0$ stuck open	1	1	1	LastZ
$N_0$ stuck short	1	$I_{DDQ}$	1	0
$N_1$ stuck open	1	1	1	LastZ
$N_1$ stuck short	1	1	$I_{DDQ}$	0

5. Test patterns are written as  $ab$

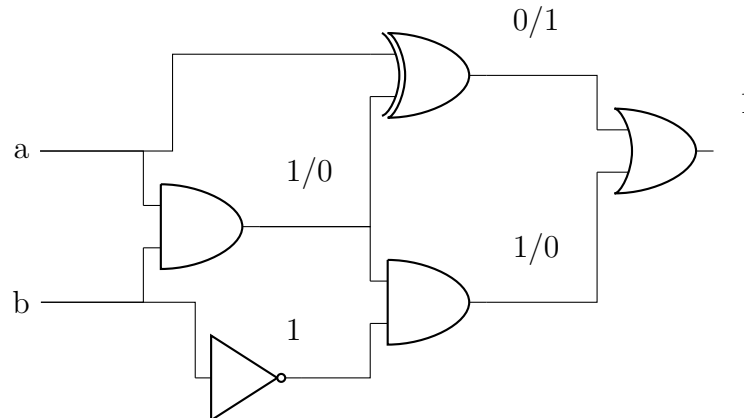- (1) Note that  $a = 1$  in order to exercise d sa0, as that is the only input that can set the wire d to 1. Also note that  $b = 0$ , as otherwise the fault d sa0 will be quenched at the OR-gate. Therefore the only input that could test this fault is 10. Here is what this input produces:



So even with this input, the fault cannot be detected. The fault is therefore redundant.


We can remove the redundancy by considering the operation of the circuit:

$$a \oplus (a + b) = a\overline{(a + b)} + \overline{a}(a + b) = a\overline{a}\overline{b} + \overline{a}a + \overline{a}b = \overline{a}b$$


$$(a + b)\overline{b} = a\overline{b} + b\overline{b} = a\overline{b}$$

$$(a \oplus (a + b)) + (a + b)\overline{b} = \overline{a}b + a\overline{b}$$

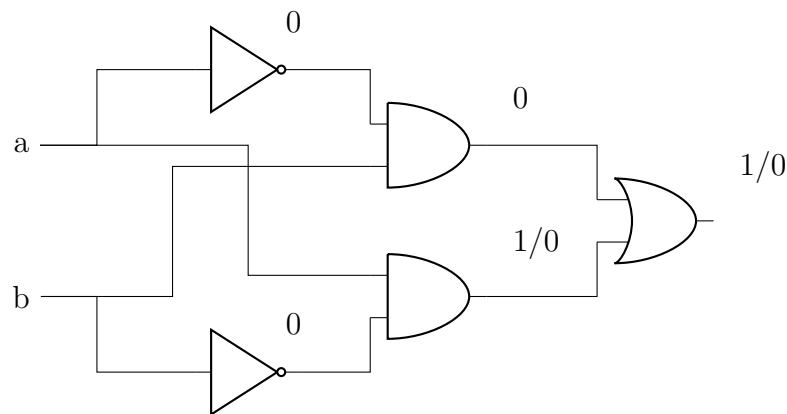We can now detect the fault using the input 11:




- (2) 10:

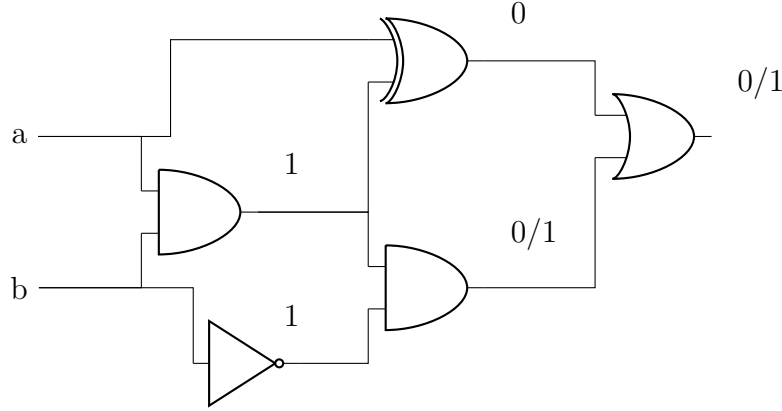

As stated above, the operation is equivalent to:

$$\bar{a}b + a\bar{b} = a \oplus b$$

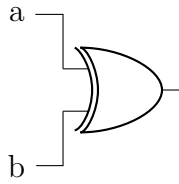Therefore, the boolean operation this circuit is equivalent to is exclusive-OR. The minimum implementation is:



6. Test patterns are written as  $abc$ .

Not that a  $*$  symbol is used where appropriate to represent the AND operation for clarity, in order to help distinguish between, for example,  $\overline{a * c}$  and  $\bar{a} * \bar{c}$

$$\begin{aligned} \text{(i)} \quad \bar{a} \frac{dz}{da} &= \bar{a}(z(a=1) \oplus z(a=0)) = \bar{a}((\bar{c} + cb) \oplus cb) \\ &= \bar{a}(\bar{c} + \overline{cbcb} + (\bar{c} + cb)\bar{cb}) = \bar{a}(\bar{c}\bar{c}bcb + \bar{c}\bar{c}\bar{b} + cb\bar{c}\bar{b}) \\ &= \bar{a} * \bar{c}cb = \bar{a} * \bar{c}(\bar{c} + b) = \bar{a} * \bar{c} + \bar{a} * \bar{c}b = \bar{a} * \bar{c}(1 + b) = \bar{a} * \bar{c} = 1 \end{aligned}$$

The patterns  $\{000, 010\}$  can detect the fault.

$$\begin{aligned} \text{(ii)} \quad h \frac{dz}{dh} &= h(z(h=1) \oplus z(h=0)) = h(1 \oplus a\bar{c}) = h\bar{a}\bar{c} = h(\bar{a} + c) \\ &= h\bar{a} + hc \end{aligned}$$

Note that  $h = cb$ .

$$h \frac{dz}{dh} = \bar{a}bc + bc = bc(a + 1) = bc = 1$$

The patterns  $\{011, 111\}$  can detect the fault.

$$\begin{aligned} \text{(iii)} \quad \bar{h} \frac{dz}{dh} &= \bar{h}\bar{a} + \bar{h}c = \bar{c}\bar{b}\bar{a} + \bar{c}bc = (\bar{c} + \bar{b})\bar{a} + (\bar{c} + \bar{b})c \\ &= \bar{a}\bar{b} + \bar{a}\bar{c} + \bar{b}c + \bar{c}c = \bar{a}\bar{c} + \bar{a}\bar{c} + \bar{b}c = 1 \end{aligned}$$

The patterns  $\{000, 001, 010, 101\}$  can detect the fault.

$$\begin{aligned}
 \text{(iv)} \quad e \frac{dz}{de} &= e(z(e=1) \oplus z(e=0)) = e((a\bar{c} + b) \oplus a\bar{c}) \\
 &= e(\overline{a\bar{c} + b}a\bar{c} + (a\bar{c} + b)\overline{a\bar{c}}) = e(\bar{b} * \overline{a\bar{c}a\bar{c}} + a\bar{c}\overline{a\bar{c}} + b\overline{a\bar{c}}) = e\bar{b}\overline{a\bar{c}} \\
 &= be(\bar{a} + c) = \bar{a}be + bec
 \end{aligned}$$

Note that  $e = c$ .

$$e \frac{dz}{de} = \bar{a}bc + bc = bc(\bar{a} + 1) = bc = 1$$

The patterns  $\{011, 111\}$  can detect the failure.

$$\text{(v)} \quad \bar{e} \frac{dz}{de} = \bar{a}\bar{b}\bar{c} + \bar{b}\bar{e}c = \bar{a}\bar{b}\bar{c} + bc\bar{c} = \bar{a}\bar{b}\bar{c}$$

The pattern  $\{010\}$  can detect the failure.

$$\text{(vi)} \quad c \frac{dz}{dc} = c(z(c=1) \oplus z(c=0)) = c(b \oplus a) = c(\bar{a}b + a\bar{b}) = \bar{a}bc + a\bar{b}c = 1$$

The patterns  $\{011, 101\}$  can detect the fault.

7. Test patterns are written as  $ab$ .

$$\text{(a)} \quad \bar{a} \frac{di}{da} = \bar{a}(i(a=1) \oplus i(a=0)) = \bar{a}(b \oplus 0) = \bar{a}b = 1$$

The pattern  $\{01\}$  can detect the fault.

$$\text{(b)} \quad \bar{d} \frac{di}{da} = \bar{d}(i(d=1) \oplus i(d=0)) = \bar{d}(ab \oplus 0) = \bar{d}ab$$

Note that  $d = a$ .

$$\bar{d} \frac{di}{da} = \bar{a}ab = 0 = 1$$

We have reached a contradiction, therefore this fault cannot be detected.

$$\text{(c)} \quad \bar{g} \frac{di}{dg} = \bar{g}(i(g=1) \oplus i(g=0)) = \bar{g}(ab \oplus 0) = \bar{g}ab$$

Note that  $g = ab$ .

$$\bar{g} \frac{di}{dg} = \bar{a}bab = 0 = 1$$

We have reached a contradiction, therefore this fault cannot be detected.

8. Below are the signatures calculated for the sequence  $M = 10011011$  (fault-free) and the faulty sequence  $M' = 11111111$

$M$	1	$x$	$x^2$	$x^3$	$M'$	1	$x$	$x^2$	$x^3$
1	0	0	0	0	1	0	0	0	0
1	1	0	0	0	1	1	0	0	0
0	1	1	0	0	1	1	1	0	0
1	0	1	1	0	1	1	1	1	0
1	1	0	1	1	1	1	1	1	1
0	0	0	0	1	1	0	0	1	1
0	1	1	0	0	1	0	1	0	1
1	0	1	1	0	1	0	1	1	0
$R$	1	0	1	1	$R$	1	0	1	1

The signatures calculated for the faulty sequence  $M'$  matches the fault-free sequence  $M$ , so this fault is not detected.